

# Verilog Wiring Tips


EE371

Omid Azizi
 
# The Problem: A Wiring Mess


Goal: We want to wire up the following structure

- Its a made-up example, but similar to a multiplier array
- Whoa! A lot of work (even for 4 bit by 4 bit)


 
# Wiring a Row

Lets break this down  
- take only one row



## **METHOD 1 - MANUAL**

```
module row(A, B, R)
  input  [3:0] A;
  input          B;
  output [3:0] R;

  block b1 (A[3], B, R[3]);
  block b2 (A[2], B, R[2]);
  block b3 (A[1], B, R[1]);
  block b4 (A[0], B, R[0]);
endmodule
```

## **METHOD 2 - VERILOG**


```
module row(A, B, R)
  input  [3:0] A;
  input          B;
  output [3:0] R;

  block b [3:0] (A, B, R);
endmodule
```

# Wiring a Row

What happened?

We instantiated all 4 blocks  
at once

 

But how did the connections  
(wiring) work?

Instantiate 4 blocks

## METHOD 2 - VERILOG


```
module row(A, B, R)
  input  [3:0] A;
  input           B;
  output [3:0] R;
```

```
  block b [3:0] (A, B, R);
endmodule
```

# Automatic Connections

CASE 1: input port expects N-bit wire and you provide N-bit wire

Then, same signal goes to all blocks

 

signal B is 1-bit  
block expects 1-bit input

So, B is connected to all blocks  
(as in diagram)

## METHOD 2 - VERILOG

```
module row(A, B, R)
  input  [3:0] A;
  input          B;
  output [3:0] R;
```

```
  block b [3:0] (A, B, R);
endmodule
```

# Automatic Connections


CASE 2: input port expects N-bit wire and you provide (M\*N)-bit wire (M is number of blocks)

Then, block 0 gets first N signals, block 1 gets next N signals, etc...

signal A is 4-bit  
block expects 1-bit input

Bits are stripped off from A as connections are made.

 So block 0 gets A[0], block 1 gets A[1], ...



## METHOD 2 - VERILOG


```
module row(A, B, R)
  input  [3:0] A;
  input          B;
  output [3:0] R;
```

```
  block b [3:0] (A, B, R);
endmodule
```

works for  
R too
 
# Automatic Connections

CASE 3: neither case 1 nor 2  
apply  
Then, Error!



## METHOD 2 - VERILOG

```
module row(A, B, R)
  input [6:0] A;
  input      B;
  output [3:0] R;
```


assume signal A was 6-bit  
block still expects 1-bit input

Then Verilog wouldn't know how to  
distribute A to the blocks...error!

```
  block b [3:0] (A, B, R);
endmodule
```
 
# Automatic Connections

What if you want to send a  
signal that is not a bus?  
Then, make it a bus!



Make a 4-bit wire so connections are  
made automatically

```
module row(A, S, B, R)
  input  [2:0] A;
  input          S;
  input          B;
  output [3:0] R;
```

```
  wire [3:0] A2 = {S,A};
```

```
  block b [3:0] (A2, B, R);
endmodule
```




# Automatic Connections

What you have learned up to now is very simple, but can save you a lot of time

- You have to make a 32x32 multiplier...
- a lot of instantiations and a lot wires
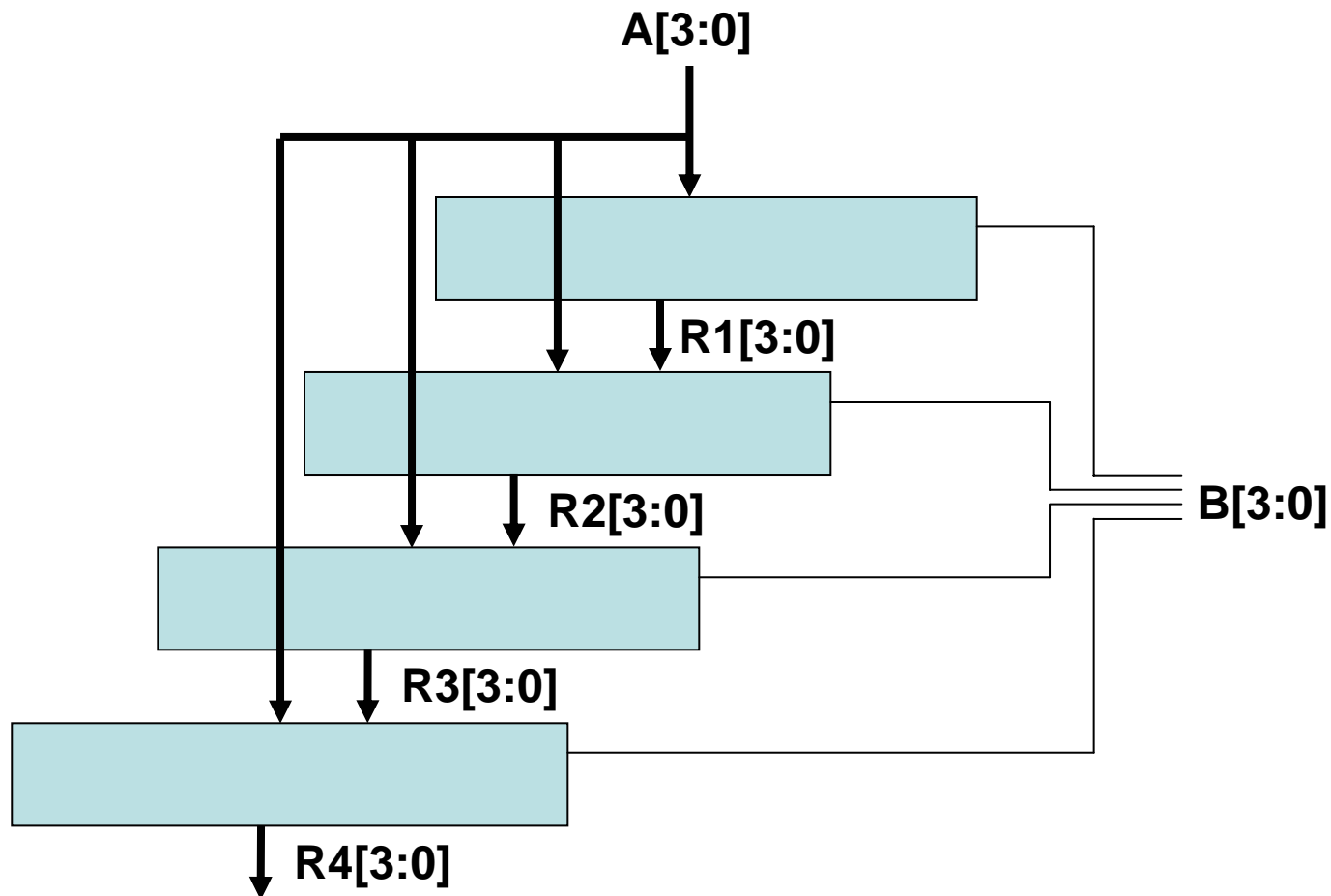
# Taking the example further


We know how to make a row, now we have to make an array



# A First Try

```
module row(A, B, Rin, Rout)
  input  [3:0] A;
  input           B;
  input  [3:0] Rin;
  output [3:0] Rout;
```


essentially same row as  
before, except now we also  
take the result of the previous  
row (Rin).



```
  block b [3:0] (A, B, Rin, Rout);
endmodule
```

```
module array(A, B, R)
  input  [3:0] A;
  input  [3:0] B;
  output [3:0] R;
```

Is it this easy now?  
What is wrong?

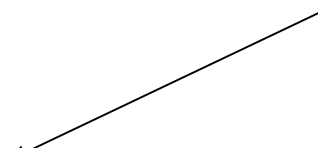

```
  row array_row [3:0] (A, B, Rin, Rout);
  assign R = Rout;
endmodule
```

# A First Try


```
module row(A, B, Rin, Rout)
  input  [3:0] A;
  input           B;
  input  [3:0] Rin;
  output [3:0] Rout;
```

```
    block b [3:0] (A, B, Rin, Rout);
endmodule
```

```
module array(A, B, R)
  input  [3:0] A;
  input  [3:0] B;
  output [3:0] R;
```

```
    row array_row [3:0] (A, B, Rin, Rout);
    assign R = Rout;
endmodule
```

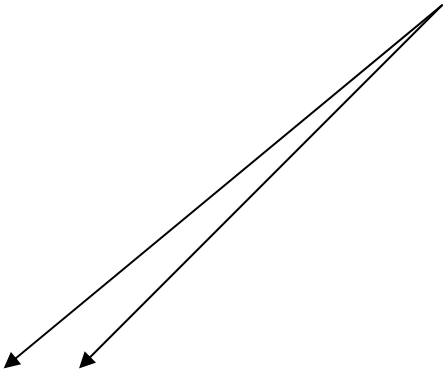A and B are hooked up correctly. All of A goes to each row (case 1). B gets distributed (case 2).



# A First Try

```
module row(A, B, Rin, Rout)
  input  [3:0] A;
  input           B;
  input  [3:0] Rin;
  output [3:0] Rout;

  block b [3:0] (A, B, Rin, Rout);
endmodule
```

```
module array(A, B, R)
  input  [3:0] A;
  input  [3:0] B;
  output [3:0] R;

  row array_row [3:0] (A, B, Rin, Rout);
  assign R = Rout;
endmodule
```

The R connections  
don't make any sense  
at all.

We want connections  
between array\_rows.

This is something new.  
Its not obvious how to  
do this. Could just give  
up and instantiate all  
rows manually, or...

# A Trick

```
module array(A, B, R)
  input  [3:0] A;
  input  [3:0] B;
  output [3:0] R;
```

```
  wire [15:0] Rin;
  wire [15:0] Rout;
```


```
  // Make Rin of one row
  // come from Rout of previous row
  // This is done with a subtle shift
```

```
  assign Rin[3:0] = 4'b0000;
  assign Rin[15:4] = Rout[11:0];
```


```
  row array_row [3:0] (A, B, Rin, Rout);
```

```
  assign R = Rout[15:12];
endmodule
```

Rin of first row is just zeros.

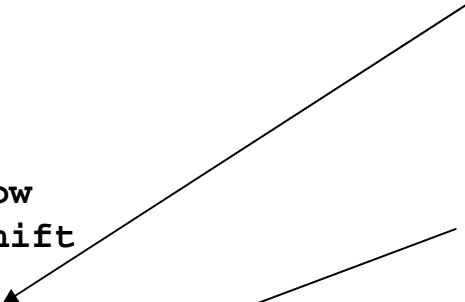

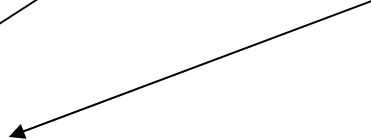Make a relationship between Rin and Rout.  
Rin of one row is Rout of previous row.



Output is Rout of last row



# A Trick

```
module array(A, B, R)
  input  [3:0] A;
  input  [3:0] B;
  output [3:0] R;

  wire [15:0] Rin;
  wire [15:0] Rout;

  // Make Rin of one row
  // come from Rout of previous row
  // This is done with a subtle shift

  assign Rin[3:0] = 4'b0000;
  assign Rin[15:4] = Rout[11:0];

  row array_row [3:0] (A, B, Rin, Rout);

  assign R = Rout[15:12];
endmodule
```

This works. And code is short.

What if we wanted to make a 64x64-bit array?

- code is just as short!

# Some Final Words

- The Verilog 2001 standard has generate statements (like VHDL):

```
generate
  genvar i;
  for (i=0; i <= 3; i=i+1) begin : u
    row array_row (A, B, R[i*4+3:i*4], R[(i+1)*4+3:(i+1)*4]);
  end
endgenerate
```

- Think of it as a preprocessor that does automatic instantiations.
- Support for generate statements may be limited since its a newer standard
- But with generate support, everything you just learned almost becomes unnecessary!